

Sintetizzare le reti logiche associate alle seguenti mappe di Karnaugh a 5 variabili, riportando le espressioni algebriche.

1)

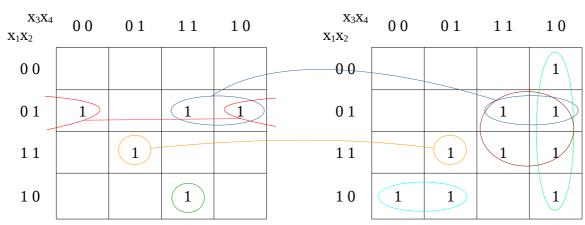

2)

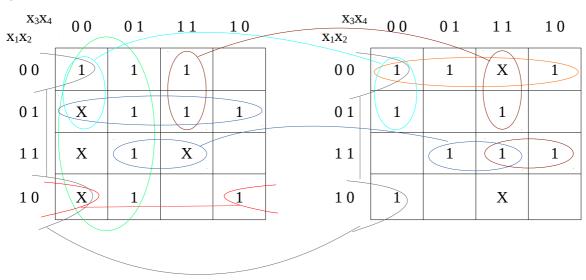

3)

X_3X_4 X_1X_2	0 0	01	11	10	X_3X_4 X_1X_2	0 0	01	11	10
0 0				X	0 0		X		
0 1	1	1		X	0 1	1	1	X	1
11	1	1	1	1	11			X	
10	X		1_		10			1	X
'		1			_				

4)

X_3X_4 X_1X_2	0 0	0 1	11	10	X_3X_4 X_1X_2	00	01	11	10
0 0		X	1		0 0	X	X	1	
0 1				1	0 1	1	1		1
11		1	X	1	11	1	1		1
10	1	1	1		10	1	1		

5)

